

Mark Scheme – Resistors & Kirchhoff's Laws

Q	Expanded Answer Guidance	Marks
1a	Kirchhoff's Current Law (KCL): <ul style="list-style-type: none"> • Total current entering a node equals total current leaving • Current in = current out • Sum of currents at a junction = 0 	1
1b	Kirchhoff's Voltage Law (KVL): <ul style="list-style-type: none"> • Sum of voltages around a closed loop = 0 • Total voltage rise equals total voltage drop 	1
1c	Ohm's Law: <ul style="list-style-type: none"> • $V = IR$ • Voltage = Current \times Resistance 	1
2a	Relationship: <ul style="list-style-type: none"> • Series resistors • Same current flows through both 	1
2b	Use the series resistance equation to work out the total resistance $R_{total} = R_1 + R_2$ $R_{total} = 2.6k + 1.8k = 4.4k\Omega$ $R_{total} = 2600 + 1800 = 4400\Omega$	1
2c	Use ohms law to work out the current through the circuit $V = IR$ $I = \frac{V}{R}$ $I = \frac{24}{4400} = 0.0054A = 540mA$	1
2d	Use power equation to work out value based on previous answers $P = I^2R$ $P = 0.0054^2 * 4400 = 0.00002916 * 4400 = 0.128304W$	2
3a	Fixed resistor: <ul style="list-style-type: none"> • Constant resistance value Variable resistor: <ul style="list-style-type: none"> • Adjustable resistance value Accept: <ul style="list-style-type: none"> • Potentiometer/rheostat examples 	2

3b	<p>Importance of power rating:</p> <ul style="list-style-type: none"> • Prevents overheating • Avoids damage • Prevents fire risk • Ensures reliability 	2
4	<p>Use voltage divider to work out value of R_2</p> $V_{out} = V_{in} * \left(\frac{R_2}{R_1 + R_2} \right)$ $2 = 10 * \left(\frac{R_2}{1000 + R_2} \right)$ $\frac{2}{10} = \frac{R_2}{1000 + R_2}$ $\frac{2}{10} (1000 + R_2) = R_2$ $200 + \frac{2}{10} R_2 = R_2$ $200 = \frac{8}{10} R_2$ $R_2 = 250$	4

5a

a)

For the resistors in parallel

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_t} = \frac{1}{1.8} + \frac{1}{1.2} = 1.39 \text{ hence,}$$

$$R_t = \frac{1}{1.39}$$

$$= 0.72 \text{ k}\Omega \text{ [B1, 1, AO2]}$$

Or, alternatively:

$$R_t = \frac{(R_2 \times R_3)}{(R_2 + R_3)}$$

$$R_t = \frac{(1.8 \times 1.2)}{(1.8+1.2)}$$

$$= 0.72 \text{ k}\Omega \text{ [B1, 1, AO2]}$$

$$V_o = \frac{R_2}{(R_1+R_2)} \times V \text{ [M1, 1, AO1a]}$$

$$V_o = \frac{0.72}{(1.6 + 0.72)} \times 240$$

$$V_o = 74.483 \text{ V or } 74.5 \text{ V [B2, 1, AO2]}$$

3

5b	<p>b)</p> <p>Calculate total resistance of the circuit: $1.6 + 0.72 = 2.320 \text{ k}\Omega = 2320 \Omega$</p> $I = \frac{V}{R}$ $I = \frac{240}{2320}$ <p>$I = 0.103 \text{ A}$ [B1, 1, AO2]</p>	1
6a	<p>Use both parallel and series resistor equations to work out total resistance</p> $\text{Parallel: } R_{tot} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$ $\text{Series: } R_{tot} = R_1 + R_2 + \dots$ $R_{tot} = 350 + \frac{1}{\frac{1}{220} + \frac{1}{120}} = 427.6470588$ <p>Use ohms law to work out the current from the source</p> $V = IR$ $I_{total} = \frac{V}{R}$ $I_{total} = \frac{24}{427.6470588} = 0.0561210453$ <p>Use the current divider equation to work out the current</p> $I_1 = I_{total} * \left(\frac{R_2}{R_1 + R_2} \right)$ $I_1 = 0.05612104539 * \left(\frac{220}{120 + 220} \right)$ $I_1 = 0.05612104539 * 0.6470588235 = 0.03631361761 \text{ A}$ $I_1 = 36.3 \text{ mA}$	3
6b	<p>Calculate the current through 220 ohm resistor</p> $I_2 = 0.05612104539 * \left(\frac{120}{120 + 220} \right) = 0.01980742778$ <p>Or</p> $I_2 = 0.05612104539 - 0.03631361761 \text{ A} = 0.01980742778$ <p>Use ohms law to work out the voltage drop</p> $V = IR$ $V = 0.01980742778 * 220 = 4.357634112$	2

7a	<p>a)</p> <p>Using parallel and series formulae:</p> $\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} \text{ and } R_T = R_1 + R_2$ <p>Series calculation</p> $R = 5.6k\Omega + 4.7k\Omega = 10.3k\Omega \text{ [B1, 1, AO2]}$ <p>Parallel calculation</p> $\frac{1}{R} = \frac{1}{10.3k\Omega} + \frac{1}{10k\Omega}$ $R = 5.07k\Omega \text{ [B2 1, AO2]}$ <p>Total resistance calculation</p> $R_t = 20k\Omega + 5.07k\Omega + 30k\Omega \text{ [M1, 1, AO2]}$ $R_t = 55.1 k\Omega \text{ [A1, 1, AO2]}$	4
7b	<p>b)</p> $I = V / R$ $I = 110 / 55,100 \text{ [M1, 1, AO1b]}$ $I = 0.002 \text{ A [A1, 1, AO1b]}$	2
8a	<p>LDR:</p> <ul style="list-style-type: none"> • Resistance changes with light intensity • Used in automatic lighting • Used in sensors 	2

8b	Thermistor: <ul style="list-style-type: none">• Resistance changes with temperature• Used in temperature monitoring• Used in thermostats	2
----	--	---